

EEE205L

Electronic Circuits I Laboratory

Lab Report

Section: 05



Group No:04

Experiment no: 04 (Software)

Name of the experiment: *Investigation of Transfer and Output Characteristics of N-Channel Enhancement MOSFET (PSPICE Simulation)*

Prepared by:

Name: Tanzeel Ahmed

ID: 24321367 Signature

Tanzeel

All Group members:

Sl.	Name	ID	Signature
1.	Esrar Ul Hossain Rafin	24121187	<i>Esrar</i>
2.	Tasmiya Tahsin Roza	24121339	<i>Tasniya</i>

Date of Submission: 26/08/2025

Objective:

To investigate the transfer and output characteristics of an N-channel enhancement MOSFET in PSPICE.

Theoretical Background:

A Metal-Oxide-Semiconductor Field-Effect Transistor (MOSFET) is a voltage-controlled semiconductor device used in both switching and amplification. In an enhancement-type N-channel MOSFET, no conductive channel exists at zero gate-source voltage (V_{GS}). When V_{GS} exceeds a certain threshold voltage (V_{TH}), electrons are attracted towards the channel region, forming a conductive path between drain and source. The drain current (I_D) increases with V_{GS} beyond V_{TH} in a nonlinear fashion. The transfer characteristics describe the relationship between V_{GS} and I_D at constant drain-source voltage (V_{DS}), allowing determination of V_{TH} . The output characteristics describe I_D variation with V_{DS} for fixed V_{GS} . In the ohmic (linear) region, I_D increases proportionally with V_{DS} . Beyond pinch-off, the MOSFET enters the saturation region where I_D remains nearly constant, making it useful for amplification. Understanding these characteristics is crucial for designing and biasing MOSFET circuits.

In modern circuit analysis, simulation is widely used to predict and study the behavior of electronic circuits before actual implementation. Simulation provides a time efficient way to test different circuit configurations and verify theoretical calculations.

PSPICE is one of the most commonly used circuit simulation tools. It allows users to design electronic circuits on a computer, apply test signals, and visualize the circuit response through graphs and plots. By simulating diode enhancement circuits in PSPICE, we can understand its characteristics without any kind of practical loss.

Problem Statement-1:

To determine the transfer characteristics (V_{GS} vs. I_D) of an N-channel enhancement MOSFET at constant $V_{DS} = 20\text{ V}$.


List of equipments:

1. Suitable computer or laptop that meets the minimum requirements
2. ORCAD Pspice Schematics software

List of equipments required in simulation:


1. Resistor (R) - 1K-ohm - 1x, 100K-ohm - 1x
2. MOSFET IRF540 - 1x
3. DC Voltage source -2x
4. Current level markers

Circuit diagram (from manual):

 

Common source configuration of N-Channel MOSFET Circuit


PSPICE Schematic diagram:

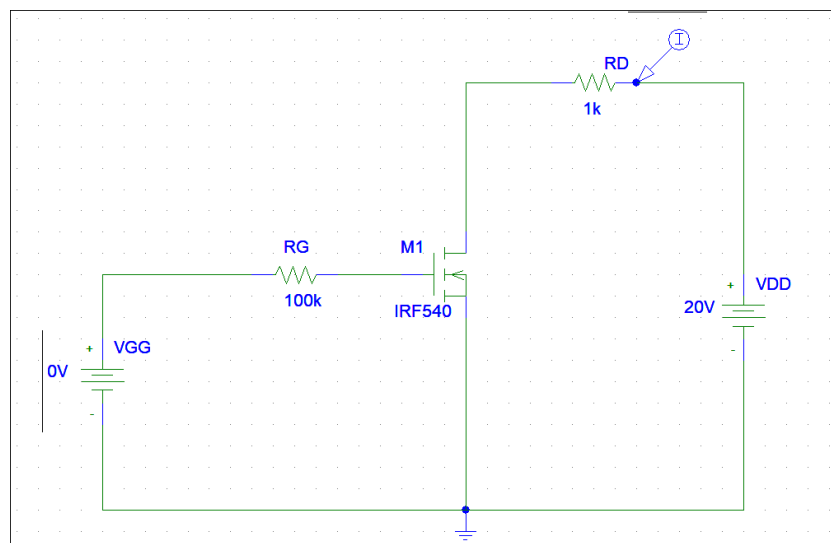


Common source configuration in simulation

PSPICE Simulation settings:

Analysis setup menu:

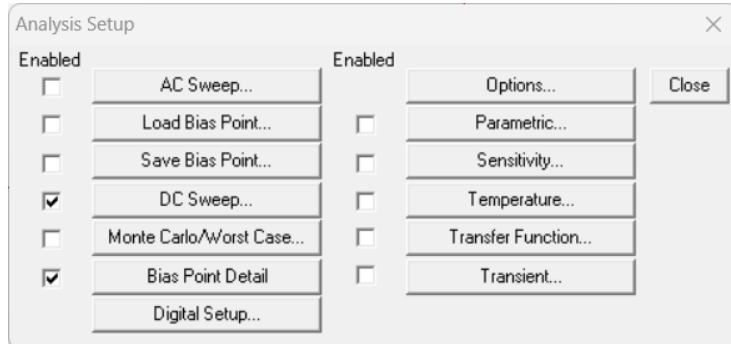


DC Sweep:

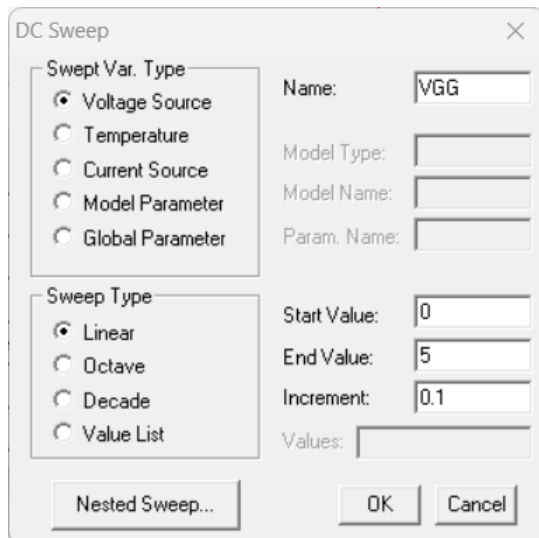


Name: VGG, Start value: 0, End value: 5, Increment: 0.1

Output waveforms:

 

Transfer characteristics simulation plot

(A) transfer_c (active)

 

Explanation: The transfer characteristics graph shows the relationship between the gate voltage and the drain current of the transistor. At lower gate voltages, the drain current stays very small in the microampere range, which represents the cut-off region of operation. Once the gate voltage crosses a threshold of around 3.1 V, the drain current increases sharply, reaching nearly 20 mA, which indicates the transistor has entered its active or saturation region. This curve highlights how the input gate voltage effectively controls the output current, demonstrating the transistor's switching behavior.


Data table (Simulated):

VGS (V)	I _D
0	44.904uA
0.5	44.904uA
1	44.904uA
2	44.904uA
3	44.904uA
3.1	87.912uA
3.2	19.692mA
3.3	19.975mA
3.4	19.991mA
3.5	19.993mA

Data table and graph (From hardware experiment):

V_{GS} (V)	V_{RD} (V)	$I_D = \frac{V_{RD}}{R_d}$ (mA)
0	0	0
0.5	0	0
1.0	0	0
1.5	0	0
2.0	0	0
2.5	0	0
2.6	0	0
2.7	0	0
2.8	0	0

2.9	0	0
3.0	0	0
3.1	0.37	0.374
3.2	0.48	0.485
3.3	2.53	2.56
3.4	4.42	4.47
3.5	11.23	11.34

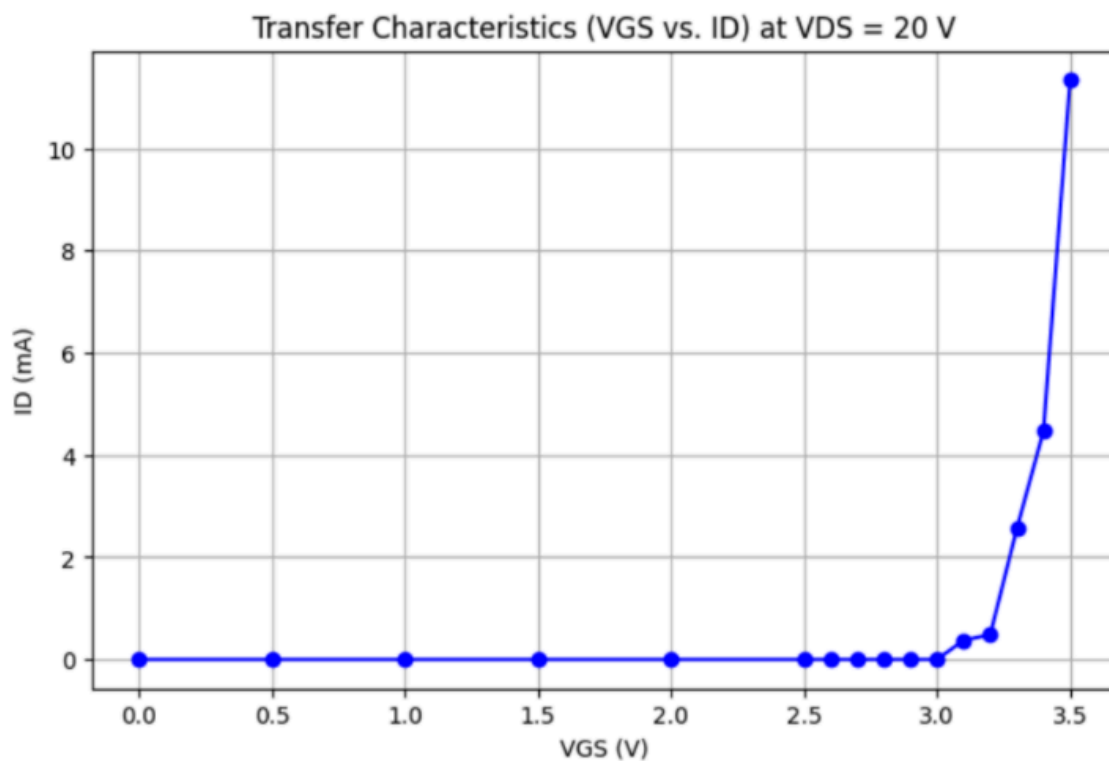

Comparison:

Simulated activation voltage 3.1V = 87.912uA

Hardware activation voltage 3.1V = 0.347mA

Difference = (0.347mA - 87.912uA) = 0.259mA

Simulated end voltage 3.1V = 19.993mA

Hardware end voltage 3.1V = 1.34mA

Difference = (19.993-11.34) = 8.653mA

Discussion:

From the plotted graph, it is evident that the MOSFET remains off until VGS reaches approximately 3.1 V. Beyond this threshold voltage ($V_{TH} \approx 3.0$ V), I_D increases sharply with VGS, showing the enhancement-mode behavior. The nonlinear rise is due to the increasing number of carriers in the channel. The difference between hardware and simulated activation point current is minimal but the 3.5V point current has a huge difference because in the lab we have external factors such as loose wiring and heat which contributes to error. Overall the simulation follows theoretical ideas so it has been successfully completed.

Problem Statement-2:

To determine the output characteristics (V_{DS} vs. I_D) of an N-channel enhancement MOSFET for $V_{GS} = 3.1$ V.

The equipment used is the same as Problem Statement-1.

The manual circuit diagram is also the same.

PSpice Schematic diagram:

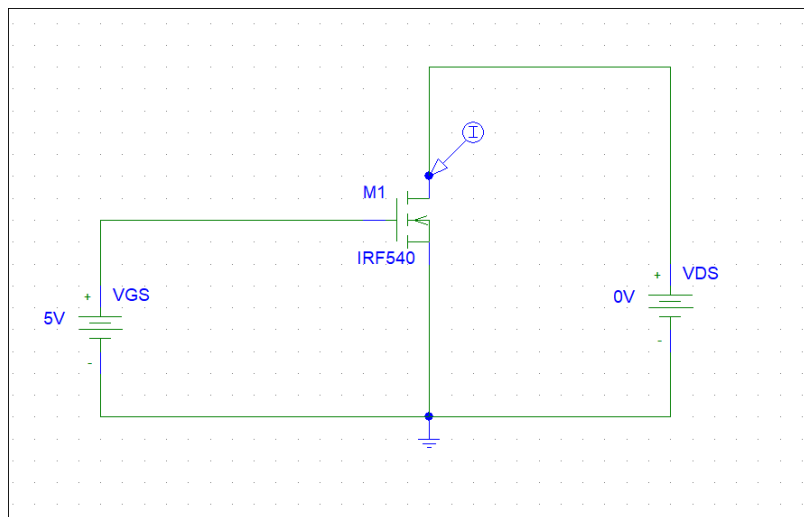



Diagram for output characteristics in simulation

PSpice Simulation settings:


Analysis setup menu:

Same as statement 1

DC Sweep with nested functionality on:

 


 Name: VDS, Start value: 0, End value: 20, Increment: 0.01



Name: VGS, Start value: 0, End value: 10 Increment: 1


Output waveforms:

 

Output characteristics simulated plot

Explanation: The graph shown is the output characteristic curve of an N-channel

(A) EX4 (active)

 

A1: (0.000,0.000) A2: (0.000,0.000) DIFF (A): (0.000,0.000)

MOSFET, where the drain current is plotted against the drain-to-source voltage for different values of gate-to-source voltage. At low, the MOSFET operates in the ohmic or linear region, where the current increases almost linearly with voltage, behaving like a variable resistor. As increases, the curves gradually flatten, indicating the transition into the saturation or active region, where I_{D1_D1D} remains nearly constant and is primarily controlled by. For small, the MOSFET remains in cutoff, showing little or no current flow, while higher values allow significantly larger drain currents, with the uppermost curve exceeding 100 A. This demonstrates the ability of the MOSFET to handle large currents and illustrates how the device shifts between cutoff, linear, and saturation regions depending on the applied voltages.


Data table (Simulated):

V_{DS} (V)	I_D
0	0
0.01	108.123mA
0.02	203.377mA
0.03	305.934mA
0.04	390.949mA
0.05	497.571mA
0.06	604.193mA
0.07	710.816mA
0.08	804.396mA
0.09	904.615mA
0.10	1.0023A
1	1.0023A
2	1.0023A
3	1.0023A

Data table and Graph (From hardware experiment):

V_{DS} (V)	V_{RD} (V)	$I_D = \frac{V_{RD}}{R_d}$ (mA)
0	0	0
.01	0.063	0.064
.02	0.096	0.098
.03	0.113	0.1141
.04	0.135	0.136
.05	0.169	0.172
.10	0.177	0.179
.30	0.184	0.186
.50	0.186	0.188
.70	0.187	0.189
1.0	0.187	0.189
2.0	0.187	0.189
3.0	0.188	0.189
4.0	0.189	0.190
5.0	0.189	0.190

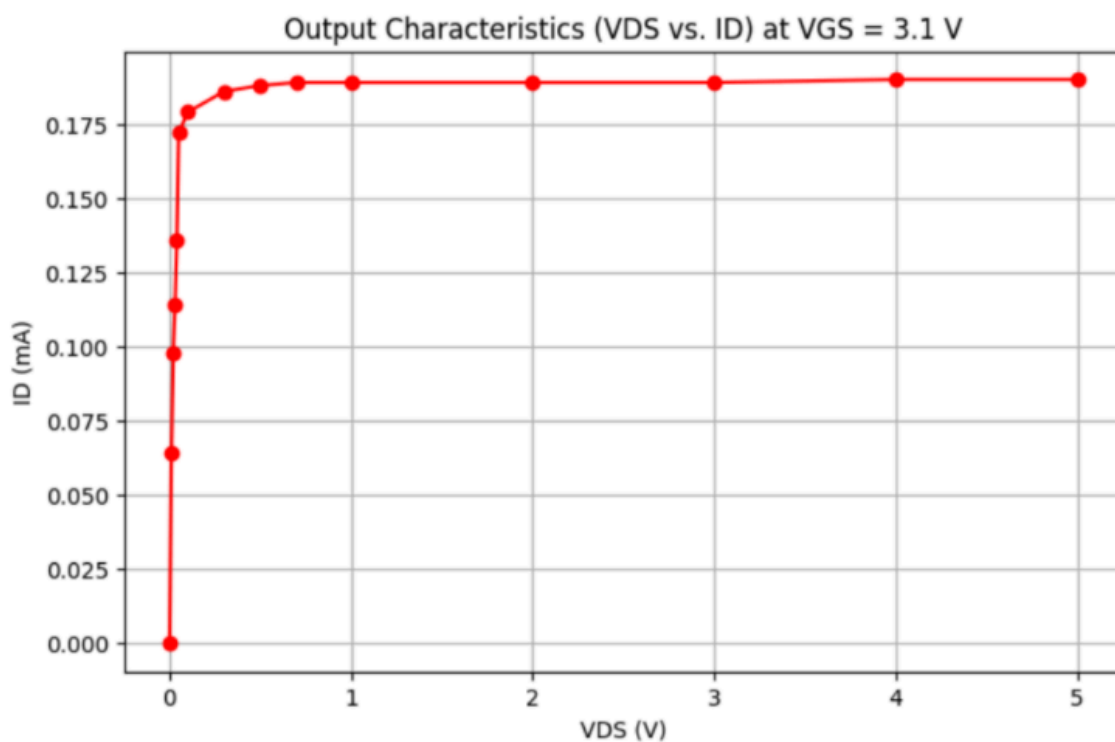3) MOSFET output characteristics curve using the data from Table 2



Comparison:

If we connect a load (resistor) like the diagram from the lab manual.

Simulated saturation voltage $0.10V = 1.0023A$

Hardware saturation voltage $0.50V = 0.188mA$

Difference = $(1.0023A - 0.188mA) = 1.002112A$

Discussion:

From the simulated graph we can see that starting from 0 to 0.09V the current increases almost proportionally but after crossing 0.10V it stays constant with 1.0023A output current. This is the starting point of the saturation region. In the lab experiment the values are different and the saturation region starts from 0.50V with an output current value hovering around 0.188 to 0.190mA. There is about 1A difference here because in the lab inaccurate resistor values, human error, power supply issues, heat and other factors contribute to loss. The simulation values align with theoretical values and the graph shows constant current so the experiment was successful.

To conclude, input and transfer characteristics simulation was completed and it helped us to learn how MOSFET's work in different electronic devices.

Drive links (.sch files): [Output and transfer characteristics](#)

EEE205L

Electronic Circuits I Laboratory

Lab Report

Section: 05



Group No: **04**

Experiment no: 05 (Software)

Name of the experiment: *Investigation of I-V characteristics of BJT (PSPICE Simulation)*

Prepared by:

Name: Tanzeel Ahmed

ID: 24321367 Signature

Tanzeel

All Group members:

Sl.	Name	ID	Signature
1.	Esrar UI Hossain Rafin	24121187	<i>Esrar</i>
2.	Tasmiya Tahsin Roza	24121339	<i>Tasmiya</i>

Date of Submission: 26/08/2025

Objective:

To measure and analyze the I-V characteristics of a BJT and determine its DC current gain (β).

Theoretical Background:

In other words a Bipolar Junction Transistor (BJT) is a three terminal semiconductor component with Emitter, Base and Collector forms in such a way that each leg makes a p-n junction. Within NPN BJT, current flows in the emitter to the lightly doped base, where they are swept to the collector hence amplifying the current. Very small base current regulates collector-emitter current much larger, and the current gain is commonly 50-500 (called β).

The transistor has 3 regions namely saturation (both junctions forward-biased), active (base-emitter forward-biased, collector-base reverse-biased), and cut off (both junctions are reverse-biased). These are input characteristics drawn by plotting base current against base-emitter voltage and output characteristics plotted by fixing base currents and observing collector current against collector-emitter voltage. There should be suitable biasing so that the active area of amplification is conducted.

In modern circuit analysis, simulation is widely used to predict and study the behavior of electronic circuits before actual implementation. Simulation provides a time efficient way to test different circuit configurations and verify theoretical calculations.

PSpICE is one of the most commonly used circuit simulation tools. It allows users to design electronic circuits on a computer, apply test signals, and visualize the circuit response through graphs and plots. By simulating BJT systems in PSpICE, we can understand its characteristics without any kind of practical loss.

Problem Statement:

Determine the input and output characteristic curves of an NPN BJT and calculate its DC current gain.


List of equipments:

1. Suitable computer or laptop that meets the minimum requirements
2. ORCAD Pspice Schematics software

List of equipments required in simulation:



1. VDC - 2x
2. Resistors of various values
3. BJT (2N222A/ZTX)
4. Voltage level and current markers

Circuit diagram (from manual):

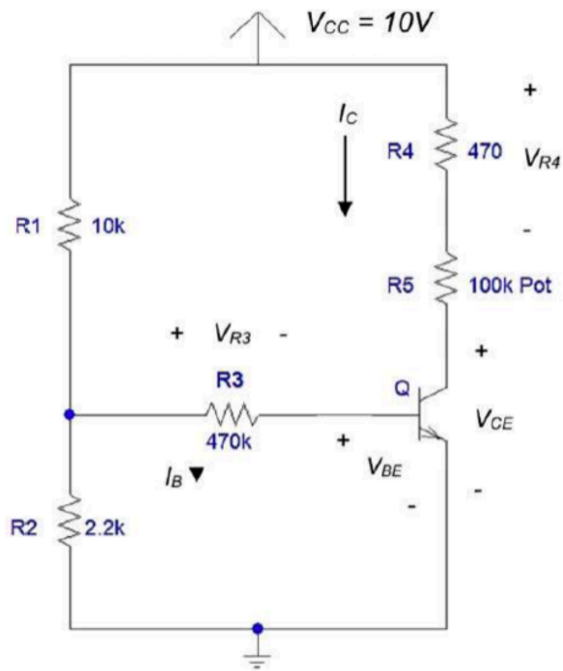

I-V investigation diagram from manual


PSPICE Schematic diagram:

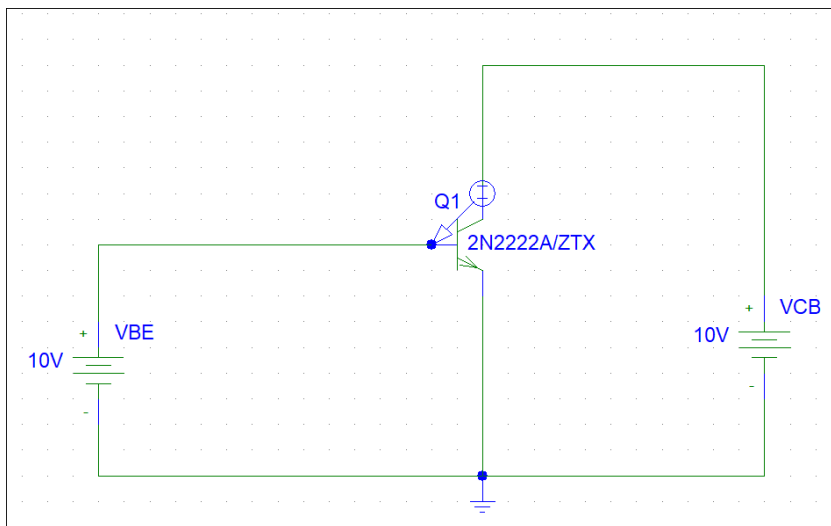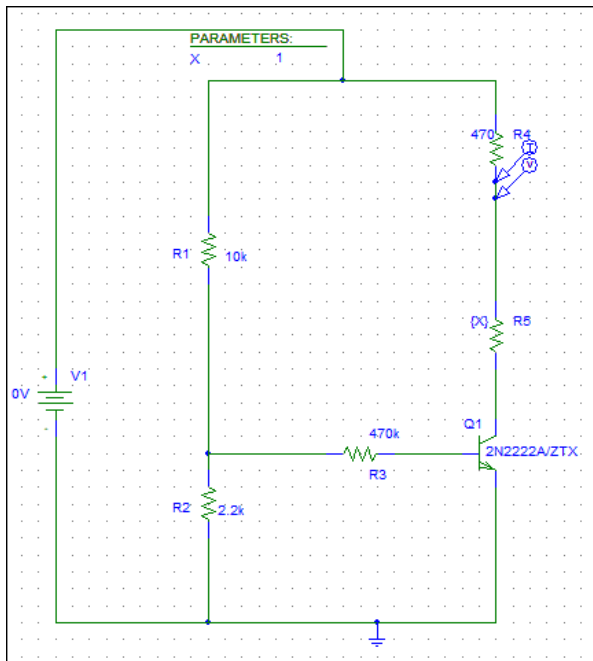


I-V Investigation diagram simulated in schematics

PSPICE Simulation settings:

Analysis setup menu:

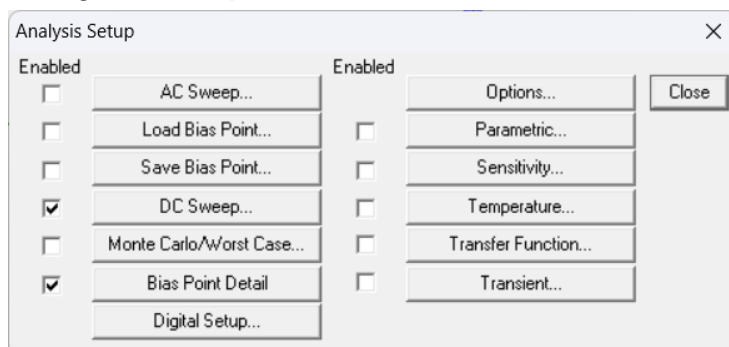

DC Sweep (For input):

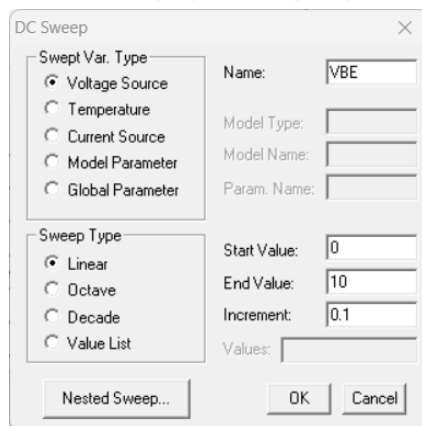


DC Sweep dialog box configuration:

- Swept Var. Type: ☒ Voltage Source, ☐ Temperature, ☐ Current Source, ☐ Model Parameter, ☐ Global Parameter
- Name: VBE
- Model Type:
- Model Name:
- Param. Name:
- Sweep Type: ☒ Linear, ☐ Octave, ☐ Decade, ☐ Value List
- Start Value: 0
- End Value: 10
- Increment: 0.1
- Values:
- Buttons: Nested Sweep..., OK, Cancel

VBE, Start 0, End 10, Increment 0.1

DC Nested Sweep (For input):

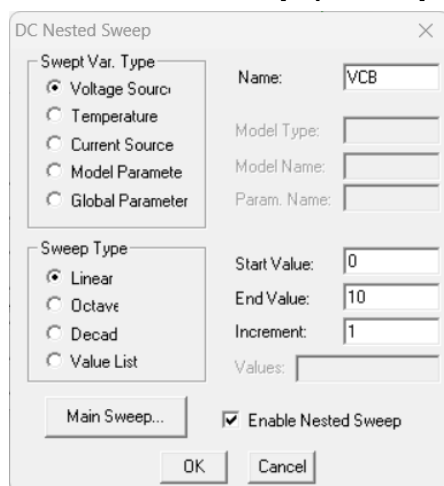


DC Nested Sweep dialog box configuration:

- Swept Var. Type: ☒ Voltage Source, ☐ Temperature, ☐ Current Source, ☐ Model Parameter, ☐ Global Parameter
- Name: VCB
- Model Type:
- Model Name:
- Param. Name:
- Sweep Type: ☒ Linear, ☐ Octave, ☐ Decade, ☐ Value List
- Start Value: 0
- End Value: 10
- Increment: 1
- Values:
- Buttons: Main Sweep..., ☒ Enable Nested Sweep, OK, Cancel

VCE, Start 0, End 10, Increment 1

Output waveforms:

 


Input characteristics plot

Explanation: The input characteristic of the BJT was obtained by sweeping VBE from 0-10 V while keeping Vce fixed at different values. The resulting graph (Fig. ...)


shows I_B increasing exponentially with V_{BE} , similar to a diode's forward conduction. At low V_{BE} (<0.6 V), the base current is negligible, indicating cutoff. As V_{BE} crosses 0.7 V, I_B rises sharply. For higher V_{BE} , the base current at a given V_{BE} is slightly larger, due to reduced base-width and the Early effect. This behavior matches the theoretical input characteristic curves of a transistor.

DC Sweep (For output:

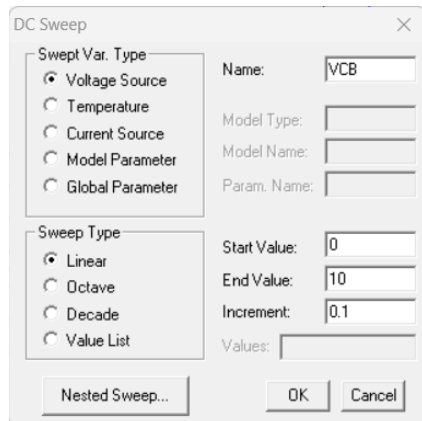


VCB, Start 0, End 10, Increment 0.1

DC Nested Sweep (For output):

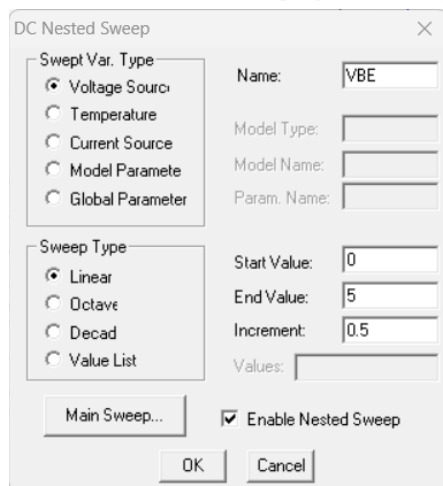



VBE, Start 0, End 10, Increment 1

 

Output characteristics plot

(A) BJTINPUT (active)

 

 

Explanation: The output characteristics of the BJT were obtained by sweeping the collector-base voltage (V_{CB}) while holding the base current (I_B) constant. The resulting graph shows a family of curves representing different base currents. In the saturation region, I_C is nearly constant and increases very slowly with V_{CB} . As V_{CB} increases, the transistor enters the active region, where I_C increases linearly with V_{CB} , and the slope of the curves becomes steeper with increasing I_B . At very high V_{CB} , the transistor enters the cutoff region, where I_C is effectively zero. These characteristics are consistent with the expected behavior of a BJT as an amplifier.

Data table (Simulated):

V_{CE} (V)	V_{R4} (mV)	$I_C = V_{R4} / R_4$ (mA)
0	0	0
0.1	123	0.26
0.2	330	0.706
0.3	340	0.72
0.4	350	0.74
0.5	347	0.745
0.6	348	0.745
0.7	348	0.745
0.8	350	0.7490
0.9	349	0.747
1	350	0.749
2	354	0.758
3	357	0.728
4	359	0.749
5	360	0.743
6	361	0.779
7	364	0.783
8	366	0.78

9	368	0.79
10	370	0.79

Data table (From hardware experiment):

Table-1:

R_3 (k Ω)	V_{R3} (V)	$I_B = V_{R3} / R_3$ (μ A)
471	✓ 1.22	2.59×10^{-6}

Table-2:

R_4 (k Ω)	V_{CE} (V)	V_{R4} (mV)	$I_C = V_{R4} / R_4$ (mA)
0.467	0.1	0.03 ✓	6.42×10^{-5}
	(0.101) 0.1	138 ✓	0.296
	(0.202) 0.2	356 ✓	0.762
	(0.312) 0.3	369	0.790
	(0.407) 0.4	372	0.797
	(0.501) 0.5	372	0.799
	(0.608) 0.6	374	0.801
	(0.697) 0.7	374	0.801
	(0.812) 0.8	375	0.803
	(0.894) 0.9	376	0.805
	(1.07) 1	376	0.805
	(2.03) 2	382	0.818

(3.17) 4	0.383	0.82
(3.98) 4	385	0.824
(5.14) 5	387	0.829
(6.03) 6	391	0.837
(6.97) 7	393	0.841
(8.14) 8	395	0.846
(9.01) 9	398	0.852
(9.6) 10	399	0.854

Comparison:

Random points have been taken for comparison

Simulated starting $I_c = 0$

Hardware starting $I_c = 6.42 \times 10^{-5}$

Simulated I_c at 0.5V = 0.745

Hardware $I_c = 0.799$

Difference = $(0.799 - 0.745) = 0.054 \text{mA}$

Simulated I_c at 5V = 0.743

Hardware $I_c = 0.829$

Difference = $(0.829 - 0.743) = 0.086 \text{mA}$

Simulated I_c at 10V = 0.79

Hardware $I_c = 0.829$

Difference = $(0.829 - 0.79) = 0.039 \text{mA}$

Discussion:

From the comparison of simulated and hardware results, it is observed that the measured collector current (I_c) values are consistently slightly higher than the simulated values across all test points. At $V_o = 0.5, \text{V}$, the hardware current was 0.799, mA compared to the simulated 0.745, mA, while at $V_{cg} = 5 \text{V}$ the hardware result was 0.829, mA against 0.743, mA. Similarly, at $V_{cg} = 10, \text{V}$, the hardware current was 0.829, mA compared to the simulated 0.790, mA. The deviations remain small, ranging between 0.039 mA and 0.086 mA, indicating that while the practical transistor exhibits slightly higher current, the overall trends and behaviors between hardware and simulation closely agree. These differences can be attributed to factors such as parasitic resistances, component tolerances, and temperature effects in real devices, which are not fully captured in the idealized simulation model.

Drive links (.sch files): [EX5](#)

EEE205L

Electronic Circuits I Laboratory

Lab Report

Section: 05



Group No: **04**

Experiment no: 06 (Software)

Name of the experiment: *Implementation of Common Emitter BJT Amplifier Circuits (PSpice Simulation)*

Prepared by:

Name: Tanzeel Ahmed

ID: 24321367 Signature

Tanzeel

All Group members:

Sl.	Name	ID	Signature
1.	Esrar UI Hossain Rafin	24121187	<i>Esrar</i>
2.	Tasmiya Tahsin Roza	24121339	<i>Tasniya</i>

Date of Submission: 26/08/2025

Objective:

Objective: The aim of the experiment is to explore the common emitter amplifier and find its gain, input and output impedance.gain (β).

Theoretical Background:

Bipolar transistors have two junctions namely the emitter-base and collector-base. When operating at high frequencies the corresponding capacitances start to have a significant effect on the operation of the devices; at low-band and mid-band frequencies can be ignored at the expense of minimal transistor performance.

In modern circuit analysis, simulation is widely used to predict and study the behavior of electronic circuits before actual implementation. Simulation provides a time efficient way to test different circuit configurations and verify theoretical calculations.

PSpICE is one of the most commonly used circuit simulation tools. It allows users to design electronic circuits on a computer, apply test signals, and visualize the circuit response through graphs and plots. By simulating BJT systems in PSpICE, we can understand its characteristics without any kind of practical loss.

Problem Statement:

This experiment investigates the common emitter amplifier's performance by measuring its current gain (β), input impedance, and output impedance at low-band and mid-band frequencies using an n-p-n transistor


List of equipments:

1. Suitable computer or laptop that meets the minimum requirements
2. ORCAD Pspice Schematics software

List of equipments required in simulation:


1. VSIN - 1x
2. VDC - 1x
3. Capacitors of various values
4. Resistors of various values
5. BJT (2N222A/ZTX)
6. Voltage level markers

Circuit diagram (from manual):

 

Common emitter BJT amplifier circuit


PSPICE Schematic diagram:

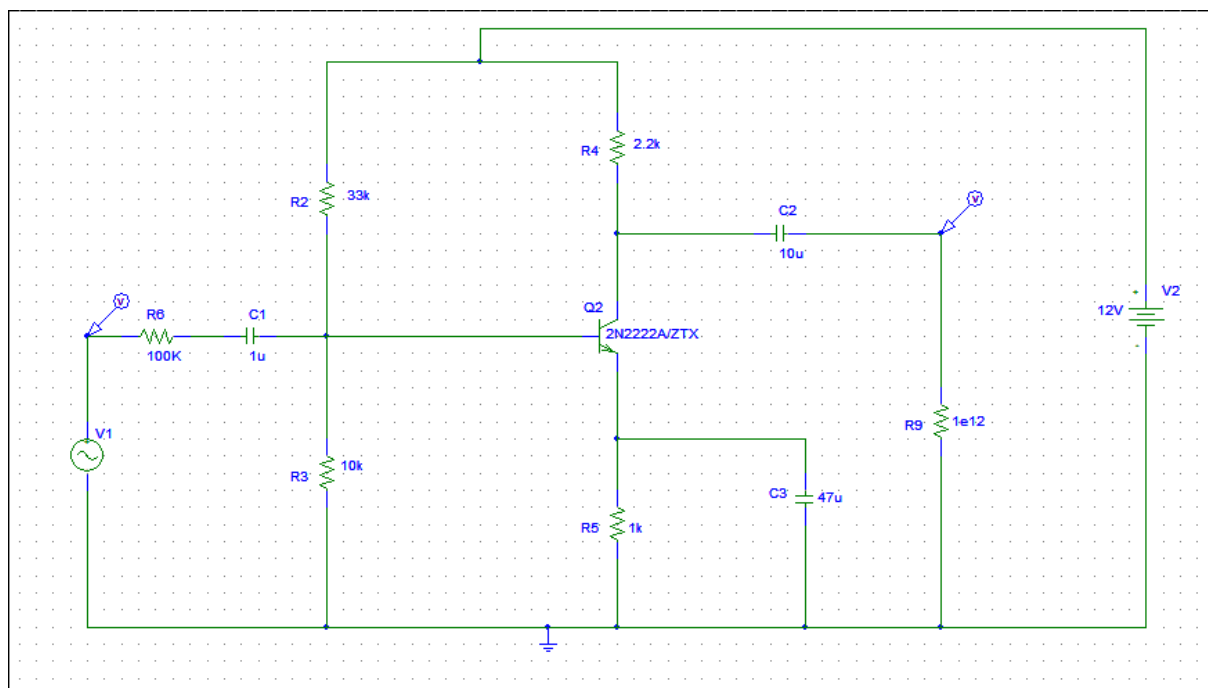


Common emitter BJT amplifier circuit in simulation

PSPICE Simulation settings:

Analysis setup menu:

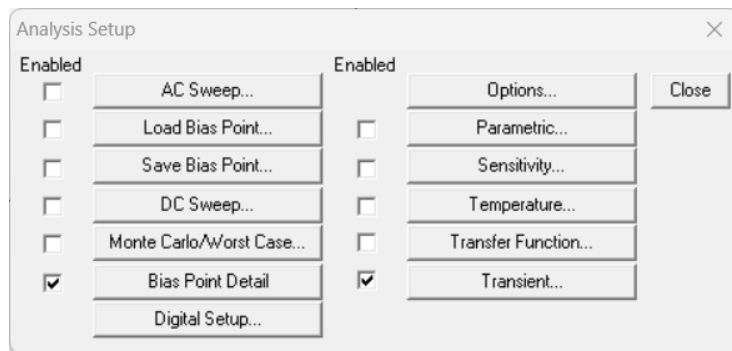


Transient:

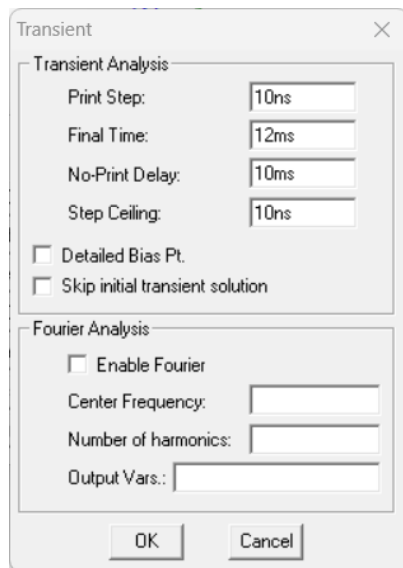


Print step 10ns, Final time 12ms, No-print delay 10ms, Step Ceiling 10ns

VSIN:

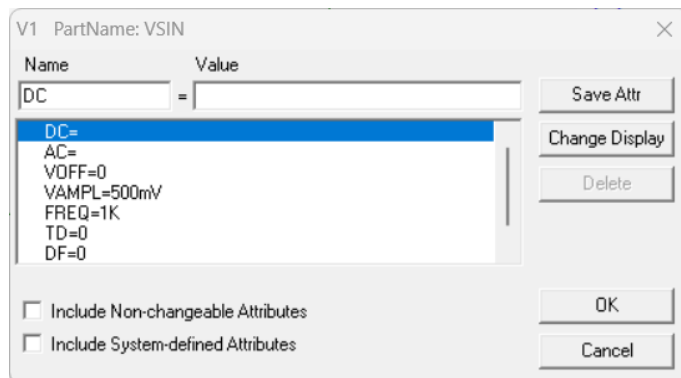


VOFF=0, VAMPL=500mV. FREQ=1K

(A) bjt (active)

 

Output waveforms:

 

Data table (Simulated):

Amplification $V_i = 5.11\text{mV}$

$V_o = 733\text{mV}$

(Reason: the $100\text{ k}\Omega$ input resistor and $1\text{ }\mu\text{F}$ coupling cap drop the 0.5 V source to $\sim 5.1\text{ mV}$ at the base;
small-signal gain $\approx -R_C / (r_e + (R_5 \parallel X_{C3})) \approx -2200 / (11.96 + 3.39) \approx -143.5$.)

Input impedance R_i

$V_i = 5.11\text{mV}$

$V_s = 500\text{mV}$

$R = 100\text{k-ohm}$ (series source resistor)

$$\bullet \quad R_i = R \frac{V_i}{V_s - V_i} \approx 100\,000 \times \frac{0.00511}{0.500 - 0.00511} \approx 1.03\text{ k}\Omega$$

(Consistent with $r_\pi \parallel (R_2 \parallel R_3)$: with $I_C \approx 2.09\text{ mA} \Rightarrow r_e \approx 11.96\text{ }\Omega$, $\beta \approx 100 \Rightarrow r_\pi \approx 1.20\text{ k}\Omega$;
 $R_2 \parallel R_3 \approx 7.67\text{ k}\Omega$; hence $R_i \approx 1.04\text{ k}\Omega$.)

Output Impedance R_o

- $R_o \approx R_C + |X_{C2}|$ at 1 kHz (load $\approx \infty$ via R_9)
- $|X_{C2}| = \frac{1}{2\pi f C_2} \approx \frac{1}{2\pi(1000)(10\text{ }\mu\text{F})} \approx 15.9\text{ }\Omega$
- $R_o \approx 2.2\text{ k}\Omega + 15.9\text{ }\Omega \approx \mathbf{2.22\text{ k}\Omega}$

Data table (From hardware experiment):

1. Amplification :

$V_i = 14.6 \text{ mV}$ $V_o = 3.16 \text{ mV}$

2. Input Impedance, R_i :

$V_i = 14.6 \text{ mV}$ $V_s = 500 \text{ mV}$

$R = 100.3 \text{ k}\Omega$ $R_i = 3.017 \text{ k}\Omega$

3. Output Impedance, R_o :

$R_o = 2.49 \text{ k}\Omega$

$(A_v) = v_i$

$V_i = V_s \frac{R_i}{R_s + R_i}$

$\frac{1}{v_i} = \frac{1}{V_s} \left(\frac{R_s}{R_i} + 1 \right)$

$\frac{R_s}{R_i} = \frac{V_s}{V_i} - 1$

$R_i = \frac{R_s}{\frac{V_s}{V_i} - 1}$

Asb
22.07.25

Faculty Signature and Date

Comparison:

Most of the data doesn't match with the software experiment because in simulation, an extra load resistor $1\text{e}12$ was added so the software shows an output plot. This was done in our simulation class because without this resistor, there was a flatline output.

Discussion:

The PSPICE simulation of the common emitter amplifier confirmed its amplification property, where a small input signal of 5.11 mV was amplified to about 733 mV . The input impedance was calculated using the source resistance and voltage division, while the output impedance was estimated from the circuit response. However, differences were found when comparing the simulated and hardware results, mainly because an additional large load resistor ($1\text{e}12 \Omega$) was used in the simulation to obtain a proper output waveform. This adjustment, along with the idealized conditions of simulation, explains the mismatch with practical data. Overall, the experiment successfully demonstrated the operation of a common emitter amplifier and the value of using PSPICE for circuit analysis before implementation.

Drive links (.sch files): [EXP 6 Common emitter amplifier](#)